

[Examrace: Downloaded from examrace.com \[https://www.examrace.com/\]](https://www.examrace.com/)

For solved question bank visit [doorsteptutor.com](https://www.doorsteptutor.com)

[\[https://www.doorsteptutor.com\]](https://www.doorsteptutor.com) and for free video lectures visit [Examrace](https://youtube.com/c/Examrace/)  
[YouTube Channel \[https://youtube.com/c/Examrace/\]](https://youtube.com/c/Examrace/)

## NET, IAS, State-SET (KSET, WBSET, MPSET, etc.), GATE, CUET, Olympiads etc.: Electronics MCQs (Practice\_Test 3 of 13)

Get top class preparation for competitive exams right from your home: [get questions, notes, tests, video lectures and more \[https://www.doorsteptutor.com/\]](https://www.doorsteptutor.com/) - for all subjects of your exam.

1. Consider the parallel RLC circuit having  $R = 1$ ,  $L = 1\text{H}$ ,  $C = 1\text{F}$ . What type of response will the circuit produce?
  - a. Under damped
  - b. Over damped
  - c. Critically damped
  - d. none of these

◦ Answer: a
2. How much inductance is needed to resonate at 5 kHz with a capacitance of 12nF?
  - a. 2652 H
  - b. 11.844 H
  - c. 3.333 H
  - d. 84.33 mH

◦ Answer: d
3. The difference between the half power frequencies is called the
  - a. quality factor
  - b. resonant frequency
  - c. bandwidth
  - d. cutoff frequency

◦ Answer: c
4. A parallel RLC circuit has  $C = 0.25\text{F}$  &  $L = 2\text{H}$ . The value of  $R$  which will create unity damping factor is
  - a. 1
  - b. 2
  - c. 0.5
  - d. 4

◦ Answer: b

5. A zero of the transfer function  $H(s) = 10(s + 1) / (s + 2)(s + 3)$  is at
- 10
  - 1
  - 2
  - 3
- Answer: b
6. On the Bode magnitude plot, the slope of the pole  $1 / (5 + j\omega)^2$  is
- 20 dB/decade
  - 40 dB/decade
  - 40 dB/decade
  - 20 dB/decade
- Answer: c
7. On the bode phase plot, the slope of  $1 + j10\omega - \omega^2 / 25$  is
- 45° /decade
  - 90° /decade
  - 135° /decade
  - 180° /decade
- Answer: d
8. In an electric circuit, the dual of resistance is
- conductance
  - capacitance
  - open circuit
  - inductance
- Answer: a
9. In a series RLC circuit, which of these quality factors has the steepest curve at resonance?
- $Q = 20$
  - $Q = 12$
  - $Q = 8$
  - $Q = 4$
- Answer: d

## Frequently Asked Questions (FAQs)

- how can we find resistance underdamped value when capacitance and inductance given

**(- ma...@ on 21-Apr-2023)**

*1 Answer*

For solutions to electronics questions please visit - [[Learn more at doorsteptutor](https://www.doorsteptutor.com/Exams/GATE/Electronics/)  
<https://www.doorsteptutor.com/Exams/GATE/Electronics/>]

- ma...@ on 21-Apr-2023