

[Examrace: Downloaded from examrace.com \[https://www.examrace.com/\]](https://www.examrace.com/)

[For solved question bank visit doorsteptutor.com](https://www.doorsteptutor.com)

[\[https://www.doorsteptutor.com\]](https://www.doorsteptutor.com) and for free video lectures visit [Examrace](https://youtube.com/c/Examrace/)
[YouTube Channel \[https://youtube.com/c/Examrace/\]](https://youtube.com/c/Examrace/)

NET, IAS, State-SET (KSET, WBSET, MPSET, etc.), GATE, CUET, Olympiads etc.: Electronics MCQs (Practice_Test 4 of 13)

Doorsteptutor material for competitive exams is prepared by world's top subject experts: [get questions, notes, tests, video lectures and more \[https://www.doorsteptutor.com/\]](https://www.doorsteptutor.com/)- for all subjects of your exam.

1. The action of JFET in its equivalent circuit can be represented as a
 - a. Current controlled Current source
 - b. Current controlled Voltage source
 - c. Voltage controlled Voltage source
 - d. Voltage controlled Current source

◦ Answer: d
2. A change in the value of the emitter resistance R_e in a differential amplifier
 - a. affects the difference mode gain A_d
 - b. affects the common mode gain A_c
 - c. affects both A_d and A_c
 - d. does not effect either A_d and A_c

◦ Answer: b
3. Generally, the gain of a transistor amplifier falls at high frequencies due to the
 - a. Internal Capacitance of the device
 - b. Coupling capacitor at the input
 - c. Skin effect
 - d. Coupling capacitor at the output

◦ Answer: a
4. In a common emitter, unbypassed resistor provides
 - a. voltage shut feedback
 - b. current series feedback
 - c. negative voltage feedback
 - d. positive current feedback

◦ Answer: c
5. A constant current signal across a parallel RLC circuits gives an o/p of 1.4V at the signal frequency of 3.89kHz. At the frequency of 4 kHz, the o/p voltage will be

- a. 1 V
- b. 2 V
- c. 1.4 V
- d. 2.8 V

○ Answer: b

6. Class AB operation is often used in power (large signal) amplifiers in order to

- a. get maximum efficiency
- b. Remove even harmonics
- c. Overcome a crossover distortion
- d. reducing collector dissipation

○ Answer: c

7. The bandwidth of an RF tuned amplifier is dependent on

- a. Q-factor of the tuned O/P circuit
- b. Q-factor of the tuned I/P circuit
- c. Quiescent operating point
- d. Q-factor of the O/P and I/P circuits as well as quiescent operating point

○ Answer: a

8. Most of the linear ICs are based on the two-transistor differential amplifier because of its

- a. input voltage dependent linear transfer characteristics
- b. high voltage gain
- c. high input resistance
- d. High CMMR

○ Answer: d

9. Negative feedback in an amplifier

- a. Reduces gain
- b. Increase frequency and phase distortion
- c. Reduces bandwidth
- d. Increase Noise

○ Answer: a

10. A dc power supply has no-load voltage of 30V and a full-load voltage of 25V at full-load current of 1A. Its output resistance and load regulation respectively are

- a. 5 ohm & 20%
- b. 2.5 ohm & 20%
- c. 5 ohm & 16.7%

d. 25 ohm & 16.7%

- Answer: b

Frequently Asked Questions (FAQs)

- **Need solution of electronic mcq**

(- mo...@ on 21-Apr-2023)

1 Answer

For electronics solutions please visit - [[Learn more at doorsteptutor](https://www.doorsteptutor.com/Exams/GATE/Electronics/)
[\[https://www.doorsteptutor.com/Exams/GATE/Electronics/\]](https://www.doorsteptutor.com/Exams/GATE/Electronics/)]

- mo...@ on 21-Apr-2023